

# Error Correction Method Based On The Short-Duration Offline Test

Jan Bělohoubek, Petr Fišer, Jan Schmidt

{jan.belohoubek, petr.fiser, jan.schmidt}@fit.cvut.cz

Czech Technical University in Prague  
Prague, Czech Republic

DSD 2016, Limassol – Cyprus

# Motivation

## ■ What?

- Combine time and area redundancy to achieve error-correction
- Reduce the number of required test vectors from thousands to tens

## ■ Why?

- To reduce the total system costs
- To reduce the test time and the test-hardware complexity

## ■ How?

- Employ an extremely short offline test – *short-duration offline test*
- Describe the circuit properties required for the short-duration test
- Propose special hardware structures enabling the short-duration test

# Motivation

## ■ What?

- Combine time and area redundancy to achieve error-correction
- Reduce the number of required test vectors from thousands to tens

## ■ Why?

- To reduce the total system costs
- To reduce the test time and the test-hardware complexity

## ■ How?

- Employ an extremely short offline test – *short-duration offline test*
- Describe the circuit properties required for the short-duration test
- Propose special hardware structures enabling the short-duration test

# Motivation

## ■ What?

- Combine time and area redundancy to achieve error-correction
- Reduce the number of required test vectors from thousands to tens

## ■ Why?

- To reduce the total system costs
- To reduce the test time and the test-hardware complexity

## ■ How?

- Employ an extremely short offline test – *short-duration offline test*
- Describe the circuit properties required for the short-duration test
- Propose special hardware structures enabling the short-duration test



# Motivation

## ■ What?

- Combine time and area redundancy to achieve error-correction
- Reduce the number of required test vectors from thousands to tens


## ■ Why?

- To reduce the total system costs
- To reduce the test time and the test-hardware complexity

## ■ How?

- Employ an extremely short offline test – *short-duration offline test*
- Describe the circuit properties required for the short-duration test
- Propose special hardware structures enabling the short-duration test


- The most popular solution – TMR

 


# Fundamental Ideas

## Error-Correction

- The most popular solution – TMR

 

 
- The proposed solution – *Time-Extended Duplex (TED)*




# Fundamental Ideas

## Error-Correction

- The most popular solution – TMR

 

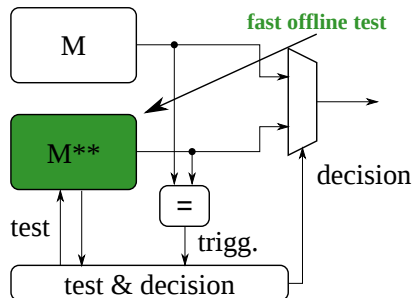
- The proposed solution – *Time-Extended Duplex (TED)*



# Fundamental Ideas

## Short-Duration Offline Test


What is required:

 



# Fundamental Ideas

## Short-Duration Offline Test

 


What is required:

- the test length in orders of tens of computational (clock) cycles only

# Fundamental Ideas

## Short-Duration Offline Test

 


What is required:

- the test length in orders of tens of computational (clock) cycles only
- 100% fault coverage

# Fundamental Ideas

## Short-Duration Offline Test

 


What is required:

- the test length in orders of tens of computational (clock) cycles only
- 100% fault coverage

→ *short-duration offline test*

# Fundamental Ideas

## Short-Duration Offline Test

 

What is required:

- the test length in orders of tens of computational (clock) cycles only
- 100% fault coverage
  - *short-duration offline test*
  - *special hardware structures*

## Observation Stuck-At-Fault Model

- Only two test vectors are required to achieve 100% fault-coverage: *all-zero* and *all-one* vector

### Theorem

*There is a two-vector-testable class of circuits with respect to the stuck-at-fault model.*

## Observation Stuck-At-Fault Model

- Only two test vectors are required to achieve 100% fault-coverage: *all-zero* and *all-one* vector


### Theorem

*There is a two-vector-testable class of circuits with respect to the stuck-at-fault model.*

Required circuit properties:

- A monotonic circuit contains no inverters  $\rightarrow$  *fault symptom* cannot change during propagation


## Observation Stuck-At-Fault Model

 

Required circuit properties:

- A monotonic circuit contains no inverters  $\rightarrow$  *fault symptom* cannot change during propagation
- The circuit conforms the *indication principle*  $\rightarrow$  every gate output is connected to at least one AND and one OR gate

## Observation Stuck-At-Fault Model

 

stuck-at-1 / fault symptom: 1  
stuck-at-0 / fault symptom: 0

Required circuit properties:

- A monotonic circuit contains no inverters  $\rightarrow$  *fault symptom* cannot change during propagation
- The circuit conforms the *indication principle*  $\rightarrow$  every gate output is connected to at least one AND and one OR gate



## Observation Stuck-At-Fault Model

- Only two test vectors are required to achieve 100% fault-coverage: *all-zero* and *all-one* vector

### Theorem

*There is a two-vector-testable class of circuits with respect to the stuck-at-fault model.*

Required circuit properties:

- A monotonic circuit contains no inverters  $\rightarrow$  *fault symptom* cannot change during propagation
  - The circuit conforms the *indication principle*  $\rightarrow$  every gate output is connected to at least one AND and one OR gate
- $\rightarrow$  Every stuck-at-fault is observable



# Efficient Monotonic Circuit Circuit Transformation

How to build the circuit complying with the “required properties”

- Make the circuit monotonic – employ *dual-rail logic*
- Reconfigurable gates – OR/AND gate
  - + less gates
  - + fault symptoms at the fault-affected wires
  - reconfigurable gate OR/AND is complex



  
# Efficient Monotonic Circuit Dual-Rail Implementation





 
## Efficient Monotonic Circuit Dual-Rail Implementation



 
## Efficient Monotonic Circuit Dual-Rail Implementation




- If the dual-rail logic serves as the inverter replacement only, the number of gates can be reduced
 
## Efficient Monotonic Circuit Dual-Rail Reduction



- If the dual-rail logic serves as the inverter replacement only, the number of gates can be reduced
- The number of gates can be the same as in the single-rail implementation (in the best case)
 
## Efficient Monotonic Circuit Dual-Rail Reduction




- If the dual-rail logic serves as the inverter replacement only, the number of gates can be reduced
- The number of gates can be the same as in the single-rail implementation (in the best case)
- Sometimes is the output polarity optional – this affects the *reduction success* → heuristics were developed



# Dual-Rail Reduction
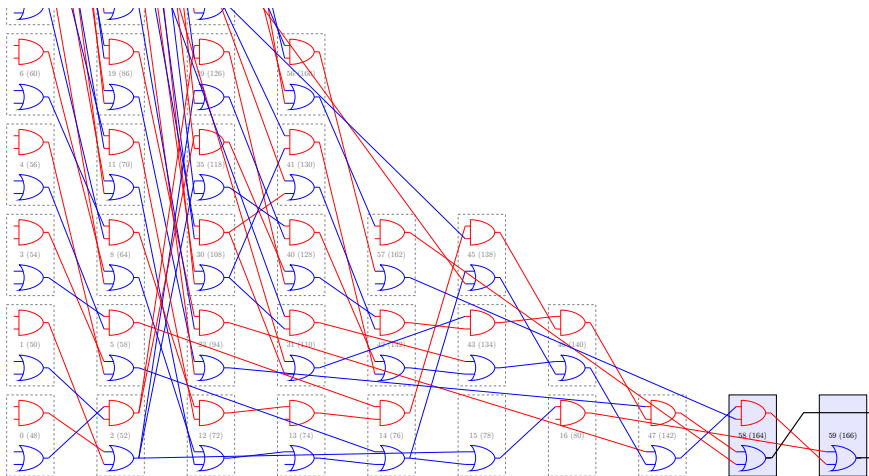
## Positive outputs only (Cordic benchmark)









# Dual-Rail Reduction

## Greedy heuristic (Cordic benchmark)

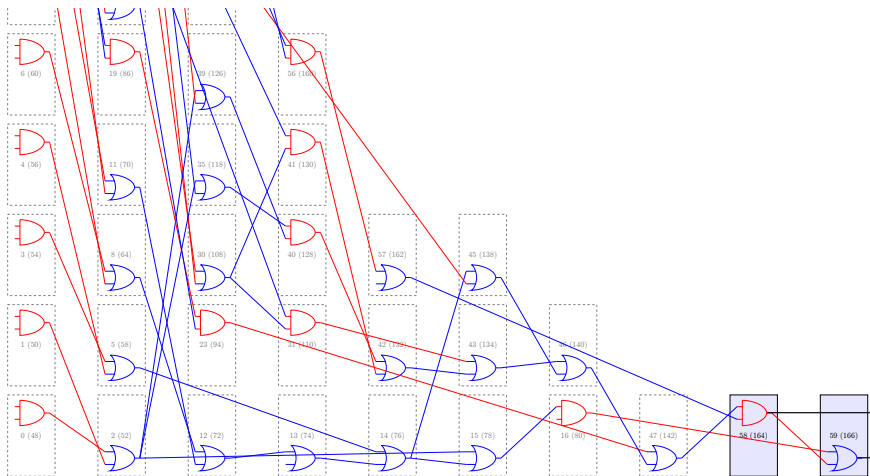



## Reconfigurable Gate Design

 


- Domino-logic AND/OR gate with increased controllability






## Reconfigurable Gate Design

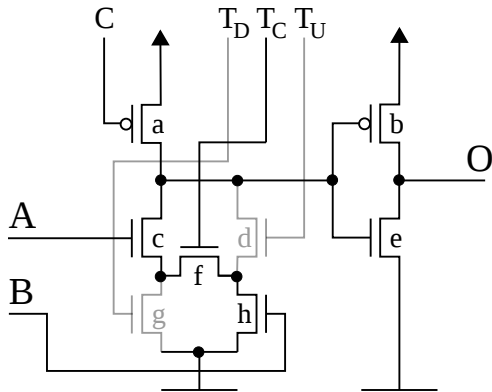

- Domino-logic AND gate  $T_D = 0$ ,  $T_C = 1$ ,  $T_U = 0$


## The Offline Test Overview

 

- Combinational logic test
- Test of the reconfiguration is required → longer test
- Inspired by two-vector-testability; uses the state-holding property and the increased controllability of dynamic gates
- Test of all *stuck-open/stuck-on* faults
- The test length remains in orders of tens computational cycles only



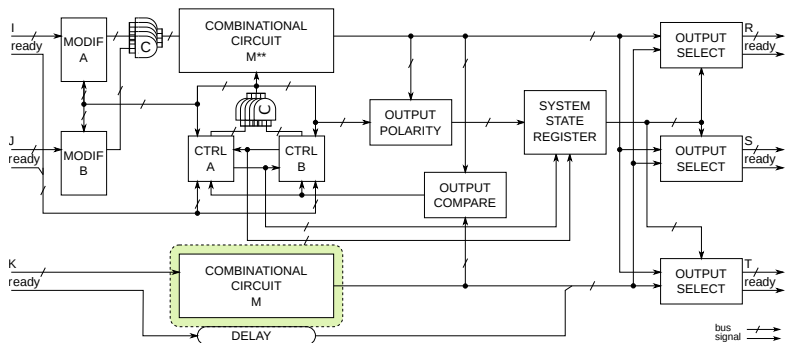
# Structure of the TED Original Combinational Part





# Structure of the TED


## Offline-Testable Combinational Part

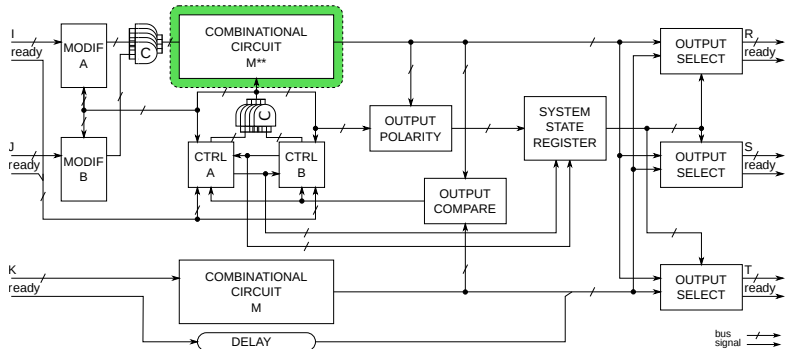



# Structure of the TED

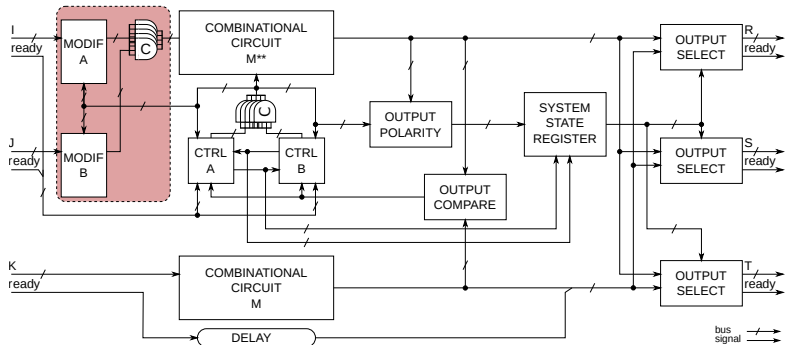
## Single-Rail to Dual-Rail and Test Input Gen.








# Structure of the TED Test Control Part

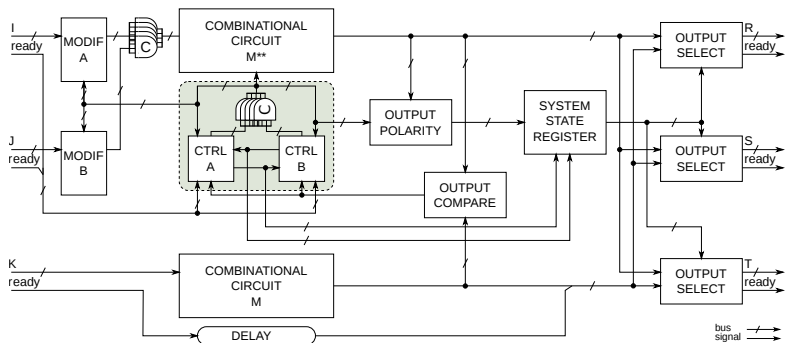




# Structure of the TED Duplex Checkers

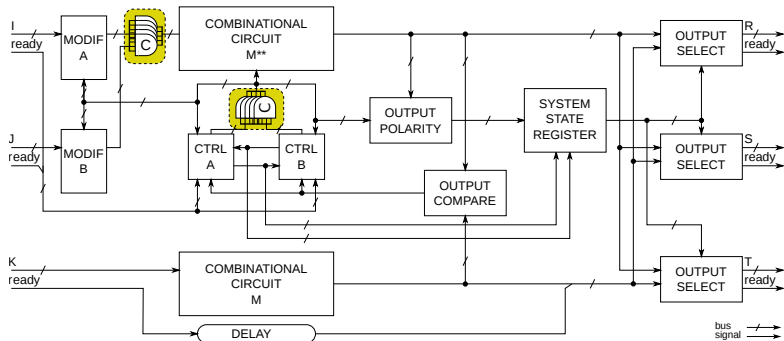



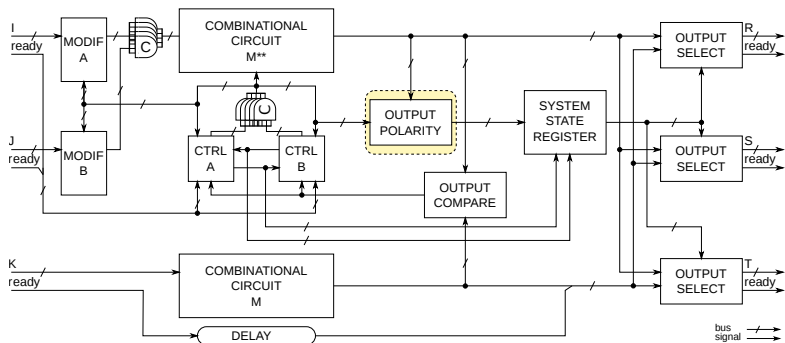
# Structure of the TED Test Response Evaluation






# Structure of the TED Test Trigger

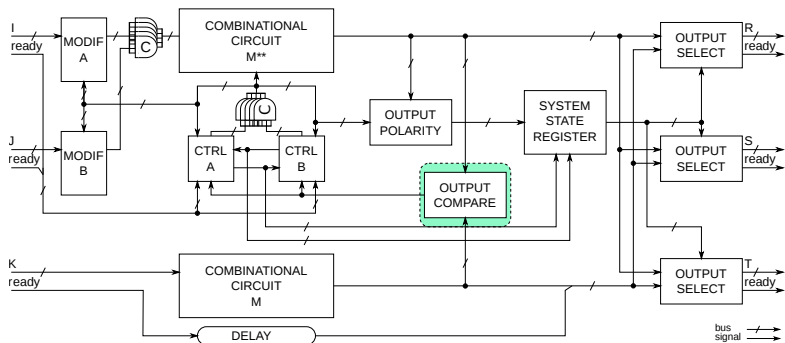




# Structure of the TED

## Last Test Results

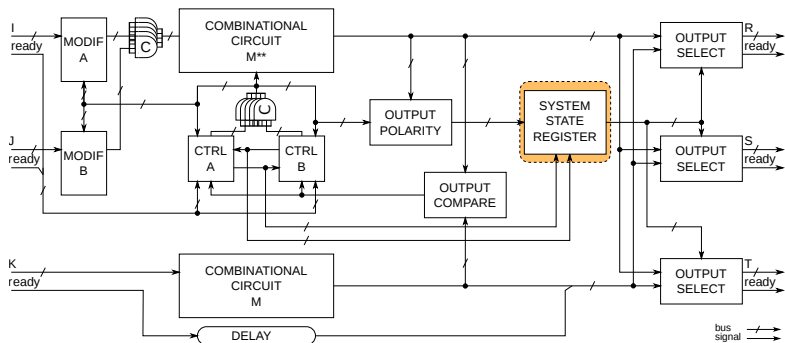



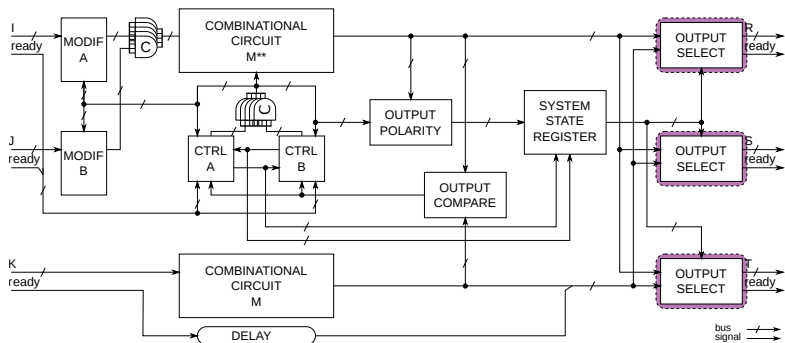
# Structure of the TED Corect Output Selection





# Offline Test in Detail

## Sub-Test 1 at Level 2

 


step	C	$T_U$	$T_C$	$T_D$	O
1	set circuit primary inputs to 0				
2	start at level $i = 1$				
3	at all levels:				↓
	0	0	0	0	
4	at level $i$ :				0
	1	1	1	1	↑
5	at level $i$ :				1
	1	0	0	0	1
6	at levels other than $i$ :				0
	1	0	1	0	0
7	set circuit primary inputs to 1				↑
8	Check if the circuit output is <i>all-one</i>				1
9	if $(++i \leq \text{depth})$ then goto 3				1



# Offline Test in Detail

## Sub-Test 1 at Level 2

 


step	C	T <sub>U</sub>	T <sub>C</sub>	T <sub>D</sub>	O
1	set circuit primary inputs to 0				
2	start at level $i = 1$				
3	at all levels:				
	0	0	0	0	↓
4	at level $i$ :				0
	1	1	1	1	↑
5	at level $i$ :				1
	1	0	0	0	1
6	at levels other than $i$ :				0
	1	0	1	0	0
7	set circuit primary inputs to 1				↑
8	Check if the circuit output is <i>all-one</i>				1
9	if $(++i \leq \text{depth})$ then goto 3				1





# Offline Test in Detail

## Sub-Test 1 at Level 2

 


step	C	$T_U$	$T_C$	$T_D$	O
1	set circuit primary inputs to 0				
2	start at level $i = 1$				
3	at all levels:				
	0	0	0	0	↓
4	at level $i$ :				0
	1	1	1	1	↑
5	at level $i$ :				1
	1	0	0	0	1
6	at levels other than $i$ :				0
	1	0	1	0	0
7	set circuit primary inputs to 1				↑
8	Check if the circuit output is <i>all-one</i>				1
9	if $(++i \leq \text{depth})$ then goto 3				1



# Offline Test in Detail

## Sub-Test 1 at Level 2

 


step	C	T <sub>U</sub>	T <sub>C</sub>	T <sub>D</sub>	O
1	set circuit primary inputs to 0				
2	start at level $i = 1$				
3	at all levels:				
	0	0	0	0	↓
4	at level $i$ :				0
	1	1	1	1	↑
5	at level $i$ :				1
	1	0	0	0	1
6	at levels other than $i$ :				0
	1	0	1	0	0
7	set circuit primary inputs to 1				↑
8	Check if the circuit output is <i>all-one</i>				1
9	if $(++i \leq \text{depth})$ then goto 3				1



# Offline Test in Detail

## Sub-Test 1 at Level 2

 


step	C	T <sub>U</sub>	T <sub>C</sub>	T <sub>D</sub>	O
1	set circuit primary inputs to 0				
2	start at level $i = 1$				
3	at all levels:				
	0	0	0	0	↓
4	at level $i$ :				0
	1	1	1	1	↑
5	at level $i$ :				1
	1	0	0	0	1
6	at levels other than $i$ :				0
	1	0	1	0	0
7	set circuit primary inputs to 1				↑
8	Check if the circuit output is <i>all-one</i>				1
9	if $(++i \leq \text{depth})$ then goto 3				1





## The Offline Test Length

 

$$(2t_e) + (dt_e) + (t_e + dt_e) + (t_e + dt_e)$$



$$t_{tot} \leq (3d + 4) \cdot t_e$$

- Classical test  $\gg 1000 \cdot t_e$
- Proposed test  $< 100 \cdot t_e$

$t_e$  – computational (clock) cycle time;  $d$  – circuit depth





# Comparison TMR vs. TED

 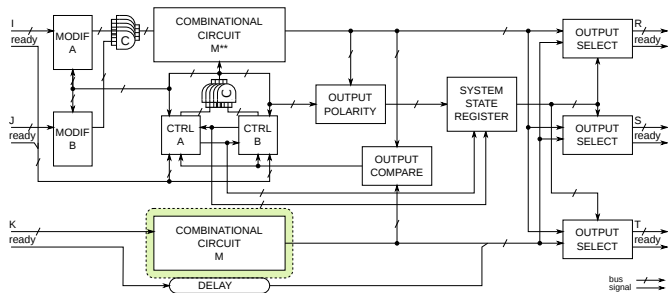





# Comparison TMR vs. TED

 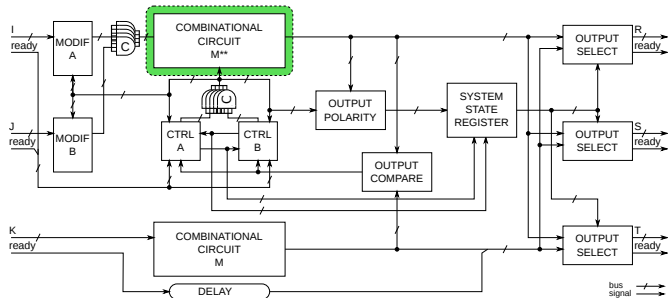





# Comparison TMR vs. TED

 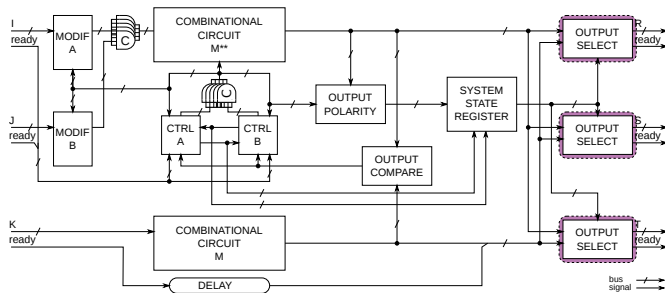






# Comparison TMR vs. TED

 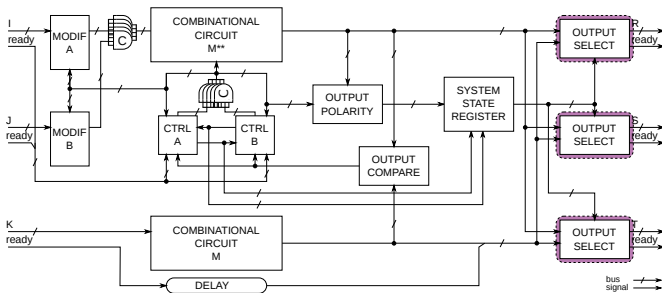

$$18 \cdot |\text{TMR SELECT}| < |M|$$


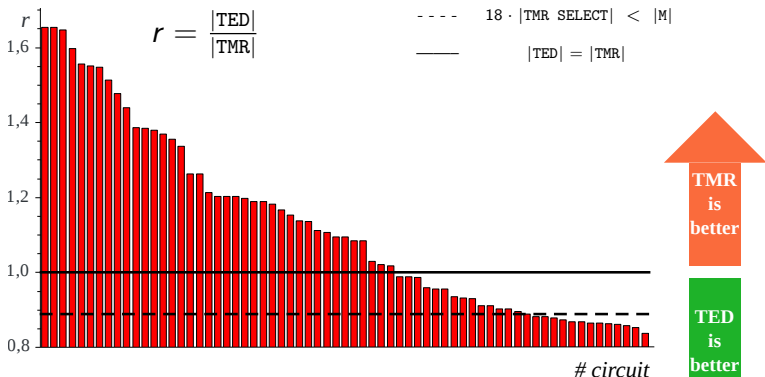
## Comparison Results (IWLS'2005 benchmark circuits)



- Based on transistor-level modeling
  - fine delay and size estimation
- TED-friendly class of circuits has been identified

## Thank you!

- The principle of the short-duration offline test was presented
- Novel gate structure allowing the offline test was introduced
- The novel error-correcting design method combining time and area redundancy was developed (TED)
- The efficient monotonic circuit implementation was presented
- Usage of the TED was suitable (compared to the TMR system) for circuits having relatively large combinational parts and small number of outputs



# What happens when ... ?

